



# Electricity & Magnetism

## Induction

### LR Post Lab

Name \_\_\_\_\_

Teacher \_\_\_\_\_

Period \_\_\_\_\_

#### Purpose

**Materials** computer and internet


[http://phet.colorado.edu/new/simulations/sims.php?sim=Circuit\\_Construction\\_Kit\\_ACDC](http://phet.colorado.edu/new/simulations/sims.php?sim=Circuit_Construction_Kit_ACDC)

**Background** Tipler Chapter 30-8

<http://hyperphysics.phy-astr.gsu.edu/hbase/electric/induct.html#c1>

#### Directions

- Construct the circuit shown below.

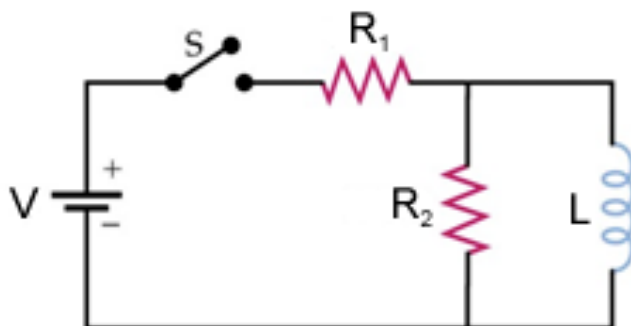

- Set the values of the circuits elements to

$$V = \underline{5 \text{ volts}}$$

$$R_1 = \underline{1 \text{ ohm}}$$

$$R_2 = \underline{4 \text{ ohms}}$$

$$L = \underline{1 \text{ henry}}$$

*Place voltmeters and ammeters in the circuit to measure the currents and voltages in step number 3*

*Place a voltage chart across  $R_2$ .*

- Experimentally determine the following:

- Case I – The switch is just closed.
- Case II – The switch is closed for a long time (time  $> 4-5 L/R$ )

	Case I	Case II
Current – $i_1$		
Current – $i_2$		
Current through Switch		
Potential – $V_1$		
Potential – $V_2$		

- Experimentally determine the voltage across  $R_2$  immediately after the switch is opened.